

Unit - 1

Digital Electronics

Logic gate :- A logic gate is a circuit design by using electronics components like diode, transistor, resistor and node. As the same employs logic gate is design to perform logical operations in digital system like computer, communication system etc. It has more than input and output.


Classification into measure types of logic gates -

① Basic logic gates -

(i) OR Gate (ii) AND Gate (iii) NOT Gate

(i) OR Gate :-

Symbol

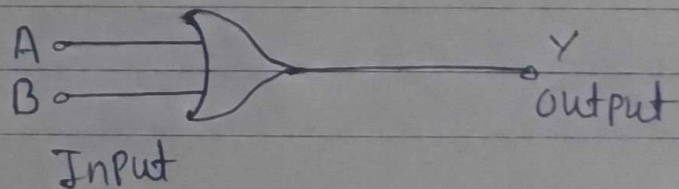

formula


$$Y = A + B$$

Truth table

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	1

(ii) AND Gate —

Symbol

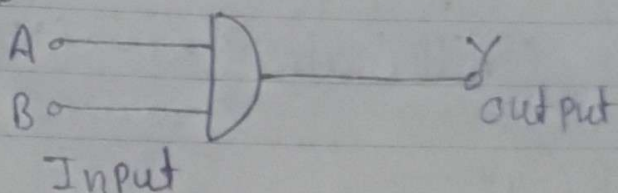

formula


$$Y = A \cdot B \quad Y = A \cdot B$$

Truth Table —

A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1

(iii) NOT Gate —

Symbol

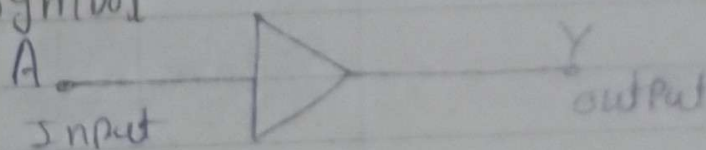

formula

$$Y = \bar{A} \quad (\text{Inverse of } A) \\ \text{opposite}$$

Truth Table


A	Y
0	1
1	0

② Universal Logic gates —

- (i) NOR Gate — (NOT + OR) Gate
 (ii) NAND Gate — (NOT + AND) Gate

(i) NOR Gate —

Symbol —

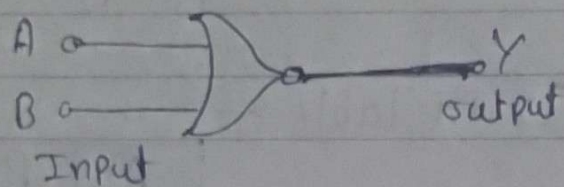

formula —


$$Y = \overline{A+B}$$

Truth Table

A	B	A+B	$Y = \overline{A+B}$
0	0	0	1
0	1	1	0
1	0	1	0
1	1	1	0

(ii) NAND Gate -

Symbol -

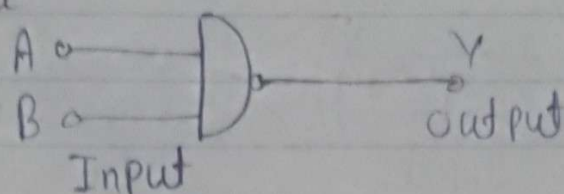

Formula -

$$Y = \overline{A \cdot B}$$

Truth Table -

A	B	$A \cdot B$	$Y = \overline{A \cdot B}$
0	0	0	1
0	1	0	1
1	0	0	1
1	1	1	0


③ Derived Logic Gate

(i) X-OR Gate

(ii) X-NOR Gate

(i) X-OR Gate -

Symbol -

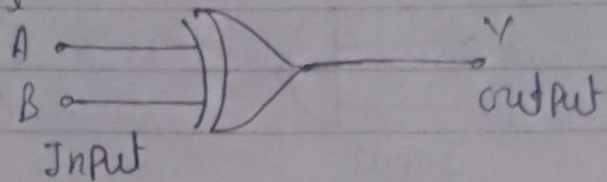

formula -

$$Y = A \oplus B$$


$$\text{or } Y = \bar{A} \cdot B + A \cdot \bar{B}$$

Truth Table -

A	B	$\bar{A} \cdot B$	$A \cdot \bar{B}$	$Y = \bar{A} \cdot B + A \cdot \bar{B}$
0	0	0	0	0
0	1	1	0	1
1	0	0	1	1
1	1	0	0	0

(ii) X-NOR Gate -

Symbol -

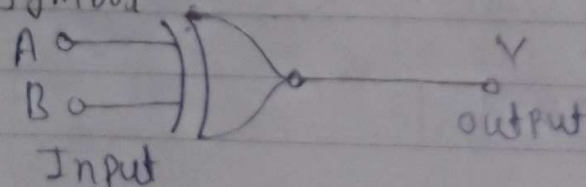

formula -

$$Y = A \odot B$$


$$\text{or } Y = \bar{A} \cdot \bar{B} + A \cdot B$$

Truth Table -

A	B	$\bar{A} \cdot \bar{B}$	$A \cdot B$	$Y = \bar{A} \cdot \bar{B} + A \cdot B$
0	0	1	0	1
0	1	0	0	0
1	0	0	0	0
1	1	0	1	1

ex-

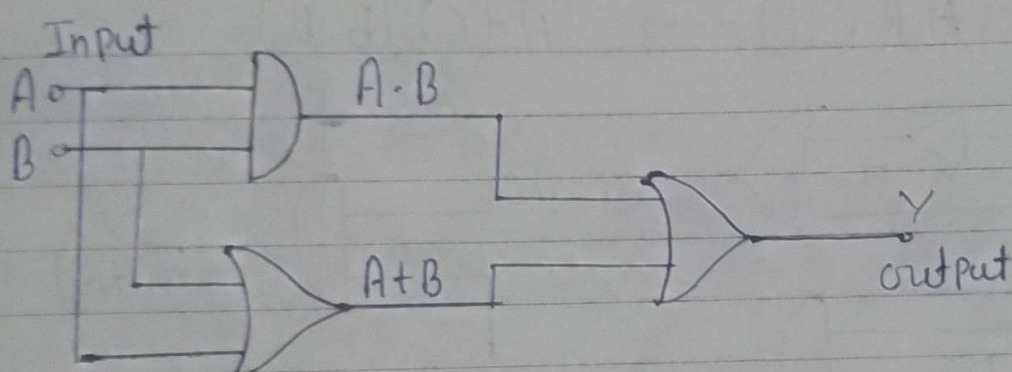① $(A, B) \longrightarrow (A \cdot B) + (A + B)$




Truth Table -


A	B	$A \cdot B$	$A + B$	$(A \cdot B) + (A + B)$
0	0	0	0	0
0	1	0	1	1
1	0	0	1	1
1	1	1	1	1

Page No. _____
Date: / /
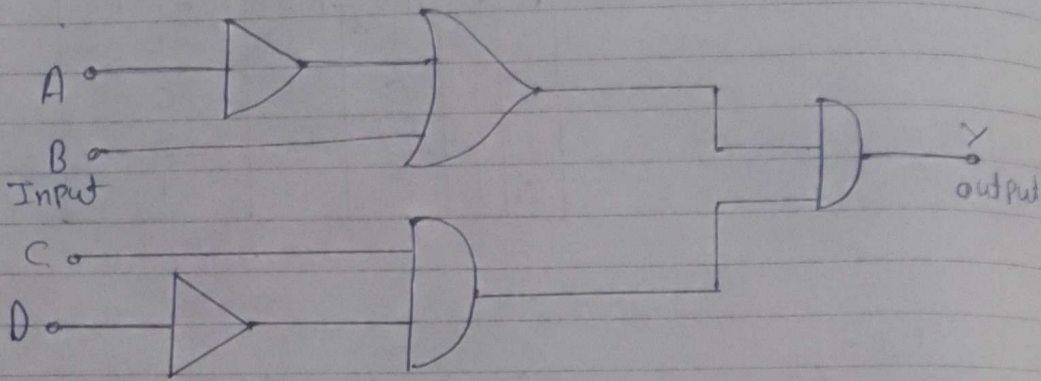
$$(2) (A, B, C, D) \rightarrow (\bar{A} + B) \cdot (C \cdot \bar{D})$$


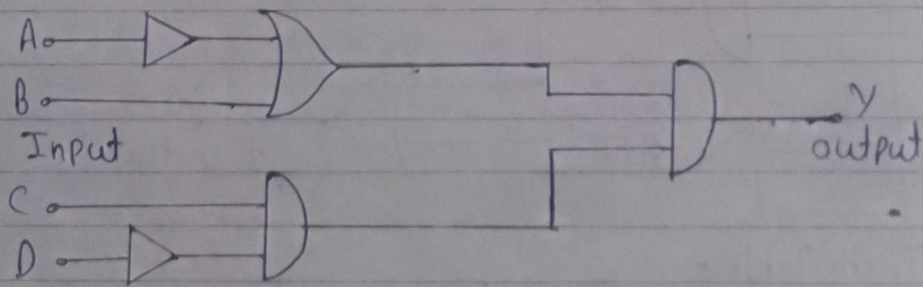
$$(3) (A, B, C, D) \rightarrow (\bar{A} + C) \cdot (B \cdot \bar{D})$$



Number System — Generally in any number system there is an ordered set of symbols called digits. which are used to specify any number the digits are defined for performing operations such as additions, subtractions, multiplications, division etc. A collection of these digits form a number which is general has two parts namely integer and fractional.

Types of number system

(i) Binary number system - (0,1).

Base - 2
numbers - 0,1

(ii) Octal number system

Base - 8
numbers - 0,1,2,3,4,5,6,7

(iii) Decimal number system

Base - 10
numbers - 0,1,2,3,4,5,6,7,8,9

(iv) Hexa Decimal number system

Base - 16
numbers - 0 to 15
Where, 10 = A, 11 = B, 12 = C, 13 = D, 14 = E and 15 = F

Q- $(48.62)_{10} = (?)_2$

Solve

$$\begin{array}{r} 48.62 \\ 1 \cdot 1 \\ \hline 48 \quad 0.62 \end{array}$$

$$\begin{array}{r|l|l} 2 & 48 & \\ \hline 2 & 24 & 0 \\ 2 & 12 & 0 \\ 2 & 6 & 0 \\ 2 & 3 & 1 \\ 2 & 1 & 1 \end{array}$$

$$48 \rightarrow 11000$$

$$0.62 \times 2$$

$$1.24 = 1$$

$$0.24 \times 2 = 0$$

$$0.48 \times 2 = 0$$

$$0.96 \times 2 = 1$$

$$0.62 = 1001$$

$$(48.62)_{10} = (11000.1001)_2$$

$$Q - (1111.1011)_2$$

$$(1111.1011)_2 =$$

$$= 1 \times 2^3 + 1 \times 2^2 + 1 \times 2^1 + 1 \times 2^0 + 1 \times 2^{-1} + 0 \times 2^{-2} + 1 \times 2^{-3} + 1 \times 2^{-4}$$

$$= 8 + 4 + 2 + 1 + \frac{1}{2} + 0 + \frac{1}{8} + \frac{1}{16}$$

$$= 15 + 0.5 + 0.125 + 0.0625$$

$$(1111.1011)_2 = (15.6875)_{10}$$

De Morgan's theorem -

(1) First theorem -

Complement of sum is equal to the product of complements

$$\overline{A+B} = \overline{A+B} \quad \overline{A} \cdot \overline{B}$$

$$\text{OR } (A+B)' = A' \cdot B'$$

(2) Second theorem

Complement of product is equal to the sum of complement

$$\overline{A \cdot B} = \overline{A+B}$$

$$\text{OR } (A \cdot B)' = A' + B'$$

Proof \Rightarrow

Inputs		Outputs			
A	B	$(A+B)'$	$(A \cdot B)'$	$A' + B'$	$A' \cdot B'$
0	0	1	1	1	1
0	1	0	1	1	0
1	0	0	1	1	0
1	1	0	0	0	0

Introduction to Semi-conductors →

Semi-conductors are materials with electrical conductivity ~~right~~ between that of conductors like metals & insulators (like ceramic & glass). They are crucial in electronics, enabling the creation of devices like transistors & of semi-conductors and integrated circuits. The conductivity of semi-conductors can be controlled making them versatile for a wide range of applications.

Key characteristics of it -

1. Intermediate conductivity - Semi-conductors have a resistivity or inverse conductivity between that of conductors and insulators, typically in the range of ten to the power of four to four ohm-cm per cm.

Energy band gap - They have a forbidden energy band gap between valence band (where electrons are ~~are~~ ~~dependent~~) and conduction band (where electrons are free to move).

Temperature dependence - The conductivity of semi-conductors is temperature dependent, increasing as temperature rises.

Charge carriers - Unlike conductors, semi-conductors don't have a constant abundance of charge carriers (e^-) at all times. They rely on external factors like temperature or light to generate or modify these carriers.

Types of Semi-conductors

- (i) Intrinsic Semi-conductors
- (ii) Extrinsic Semi-conductors

Application -

transistor, solar cells, LED, ICs etc.